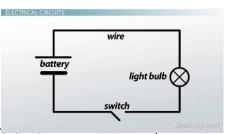


Electricity



Vocabulary

T	
Word	Meaning
Electricity	A form of energy carried by wires.
	Used for heating, lighting and to
	power machines
Electrical	Paths for moving electricity.
circuit	
Cell	A device used to generate electricity. A
	battery is a cell.
Wire	Electrical wire is used to carry
	electricity.
Motor	Changes electricity into movement.
Loop	Electricity flows, from a power source,
	in a loop or circuit back to a power
	source.
Conductor	Materials that allow electricity to flow
	through them easily
Insulator	Material that doesn't carry electricity.


Can I identify things that are powered by electricity?

Do I understand that electricity can be dangerous?

Can I construct a circuit?

Can I explain how circuits work using a circuit diagram?

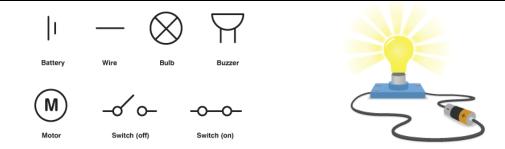Can I investigate which materials are conductors and which are insulators?



Important Facts

Electricity can be dangerous.	
Electrical energy can be converted into heat, light, sound and	
movement.	
The plastic cover that surrounds wire is an electrical insulator.	
A circuit always needs a power source.	
A circuit will only work if the loop is complete.	